

EET103 – Series Circuits Follow-Up Lecture

1) Flashlight Circuit (Cells in Series + Lamp)

- 3x AA batteries (1.5 V each) in series → 4.5 V total
- Internal resistance: 0.2 Ω per cell → 0.6 Ω total
- Lamp: ~20 Ω

Total Resistance	$R_T = 20.6 \Omega$
Current	$I = 4.5 / 20.6 \approx 0.218 \text{ A}$
Lamp Voltage	$V_{\text{lamp}} \approx 4.37 \text{ V}$
Lamp Power	$P_{\text{lamp}} \approx 0.95 \text{ W}$
Internal Loss	$P_{\text{int}} \approx 0.03 \text{ W}$

Discussion: As cells age, internal resistance increases, lamp dims. Ask students: What if r_{int} doubles?

2) Voltage Divider (Scaling 12 V to ~3.3 V)

- $R_1 = 26.7 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$
- Divider ratio: $V_{\text{out}} = V_{\text{in}} \times (R_2 / (R_1 + R_2))$

Input (V_{in})	12 V
Output (V_{out})	$\approx 3.27 \text{ V}$
Divider Current	$\approx 0.327 \text{ mA}$

Discussion: Good example for ADC scaling. What happens if $V_{\text{in}} = 14.4 \text{ V}$? How do we protect a 3.3 V ADC input?

3) Two LEDs in Series + Resistor

- Supply: 9 V battery
- LEDs: 2x red ($V_f \approx 2.0 \text{ V}$ each)
- $R = (9 - 4) / 0.015 \approx 330 \Omega$

LED Current	$\approx 15 \text{ mA}$
Resistor Power	$\approx 0.08 \text{ W}$
LED Voltage Drop	$\approx 4.0 \text{ V}$ total

Discussion: Series LEDs share current equally. What if we replace with blue LEDs ($V_f \approx 3.0 \text{ V}$ each)?