

eet103

NMC EET103 Electrical Studies I

[View the Project on GitHub](#) k2controls/eet103

EET103 Electrical Studies I

EET103 - Labs - Alternating Current & Oscilloscopes

Lab 10: Alternating Current & Oscilloscopes (with XR2206 Function Generator)

Name: _____

Objective:

- Observe the frequency range of a signal generator.
- Observe AC signals on an oscilloscope.
- Build a basic AC circuit and measure power.
- Apply Ohm's Law to AC circuits to calculate voltage, current, and power.

Materials:

- XR2206 Precise Function Signal Generator
- Multimeter
- Oscilloscope
- Scope probes
- Breadboard
- Resistors - 1K (x2)
- Speaker
- Passive buzzer

Part 1: Signal Generator - Instructor Demo


1. The instructor will demonstrate creating a 400 Hz sine wave using XR2206 signal generator and a lab oscilloscope.

2. The amplitude of the signal will be adjusted to that minimal distortion is displayed.
3. A small speaker will be connected to the signal generator sine output
 - Is a tone audible?
4. The passive buzzer will be connected to the signal generator sine output.
 - Is a tone audible?
5. The amplitude of the signal will be investigate with and without the speaker and buzzer load.
 - What does this procedure tell you about the output of the signal generator?
 - How does this behaviour compare to what you experience with a battery when loaded?
6. The speaker and buzzer tests will be reproduced using a lab function generator.
 - How is the lab function generator similar to your signal generator?
 - How is the lab function generator different than your signal generator?

Part 2: Signal Generator and Oscilloscope

1. In your own words, what is a signal generator (or function generator)?
2. Determine the frequency range of the XR2206 Precise Function Signal Generator and note the following:
 - Minimum frequency: ____
 - Maximum frequency: ____
3. What is the maximum amplitude produced by the function generator? Express and peak voltage, peak-to-peak voltage, and RMS voltage.
 - V_p : ____
 - V_{pp} ____
 - V_{RMS} : ____ (note: is this a sine wave?)
4. Describe what an oscilloscope is in your own words.
5. Explain what is meant by the setting "volts/division."

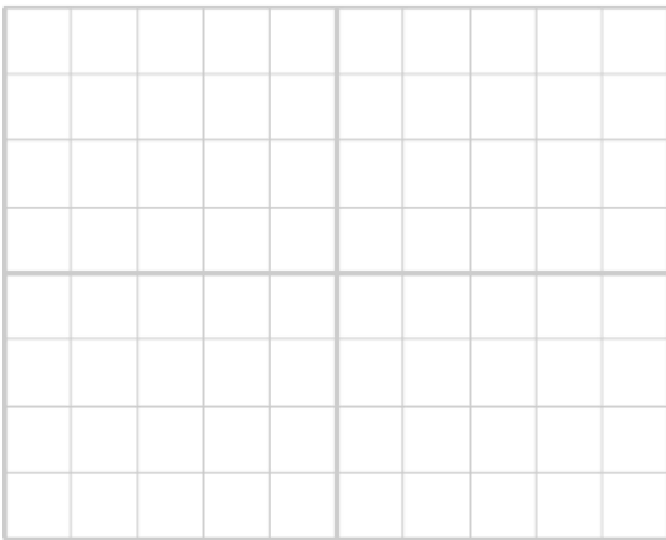6. Does changing the “volts/division” setting change the amplitude of the displayed signal?
7. Define what is meant by the setting “seconds/division.”
8. Record the make and model of the oscilloscope you are using.
9. Connect the your signal generator to the oscilloscope:
 - Set the frequency to 1000 Hz (1 kHz) and the amplitude to a peak voltage of 1 volt.
 - Sketch a rough diagram of the displayed waveform below:
 - Is there distortion at this amplitude




10. Record the following measurements from the oscilloscope:

Setting/Measurement	Value	Units
Volts/division		
Peak voltage		
Peak-to-peak voltage:		
Time Base		
Period		

11. Calculate the RMS voltage.
12. Adjust your function generator jumpers and/or connections to display square and triangular waves on your scope. Describe what changes in the waveform and what remains the same.

Part 3: Basic AC Circuit

Circuit Diagram:

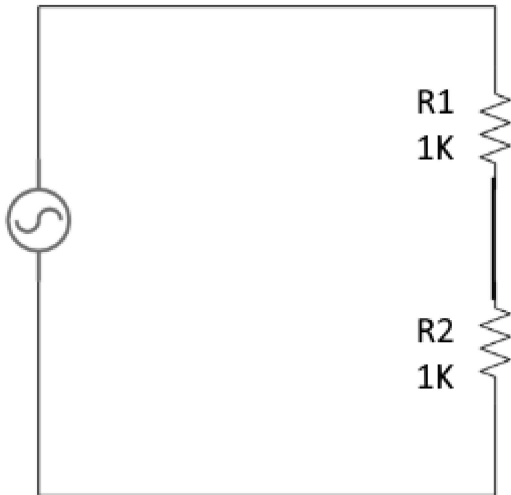

- **R1:** 1 k Ω
- **R2:** 1 k Ω
- **Signal:** 2 V peak, 1 kHz

1. Construct the circuit as shown above. Set the signal to 2 volts peak and 1 kHz.
2. Is this a series or parallel circuit?
3. Calculate the peak voltage across **R2**.
4. Calculate the RMS voltage across **R2**.
5. Using your oscilloscope:
 - Connect one channel to display the input voltage and the other to display the voltage across **R2**.
 - *Ensure both channels share a common ground and adjust the display so that both channels use the same zero voltage reference.*
6. Measure and record the peak voltage across **R2** using the oscilloscope.
7. Measure and record the RMS voltage across **R2** using the oscilloscope.
8. Measure the AC voltage across **R2** using your DMM. Does the DMM display peak or RMS voltage?
9. Calculate the RMS current through the circuit.

10. Calculate the power dissipated by **R2** using the RMS voltage and RMS current.

Part 4: Post-Lab Questions

1. What was the most challenging part of using the oscilloscope and function generator?
2. Why is it important to use RMS values of voltage and current when calculating power in an AC circuit?
3. Do Kirchhoff's voltage and current laws apply to AC circuits? Justify your answer.

This project is maintained by [k2controls](#)

Hosted on GitHub Pages — Theme by [orderedlist](#)