

Name: \_\_\_\_\_

Parts List	
Part	Quantity
555 timer	1
resistor, 100 k $\Omega$	1
resistor, 1 M $\Omega$	1
resistor, 1 k $\Omega$	1
resistor, 270 $\Omega$	1
capacitor, 5 $\mu$ F	1
capacitor, 10 $\mu$ F	1
capacitor, 100 nF	1
LED, any color	1
switch, pushbutton, NO, MC	1

**Objectives:**

- Review the datasheet for a 555 timer
- Identify the pinout for the 555 timer
- Build a monostable 555 timer circuit
- Build an astable 555 timer circuit (oscillator)
- Operate an oscilloscope to take measurements on the signal


**Section I: Prelab (Refer to the 555 timer datasheet)**

1. (3 points) Describe what an Integrated Circuit (IC) is.
2. (7 points) Complete the right column in the following table. All information is available on the datasheet.

Supply voltage ( $V_{CC}$ )	Minimum: Maximum:
Typical supply current at 5V	
Maximum power dissipation, LM555CM	
Maximum 10 second soldering temperature, PDIP package	
Trigger voltage, $V_{CC}=5V$	
Which package type are we using?	

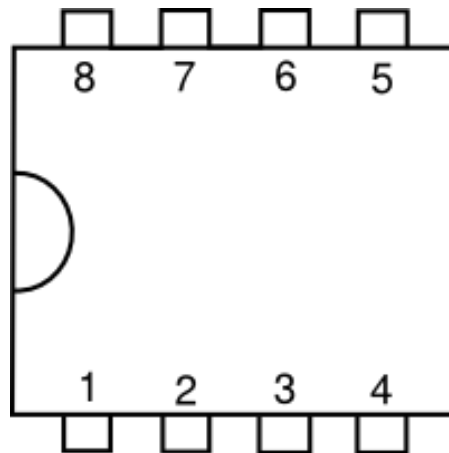3. (8 points) On the following diagram, label the pin functions for the 555 timer:


V+ (or  $V_{CC}$ )  
GND (ground)  
TR (trigger)  
DIS (discharge)  
THR (threshold)  
CV (control voltage)  
R (reset)  
OUT (output)



## Section II: Monostable

1. The following 555 circuit is for a monostable (one stable state) output. When the switch is pressed, the time on in seconds is given by

$$T_{ON} = 1.1 * RC$$

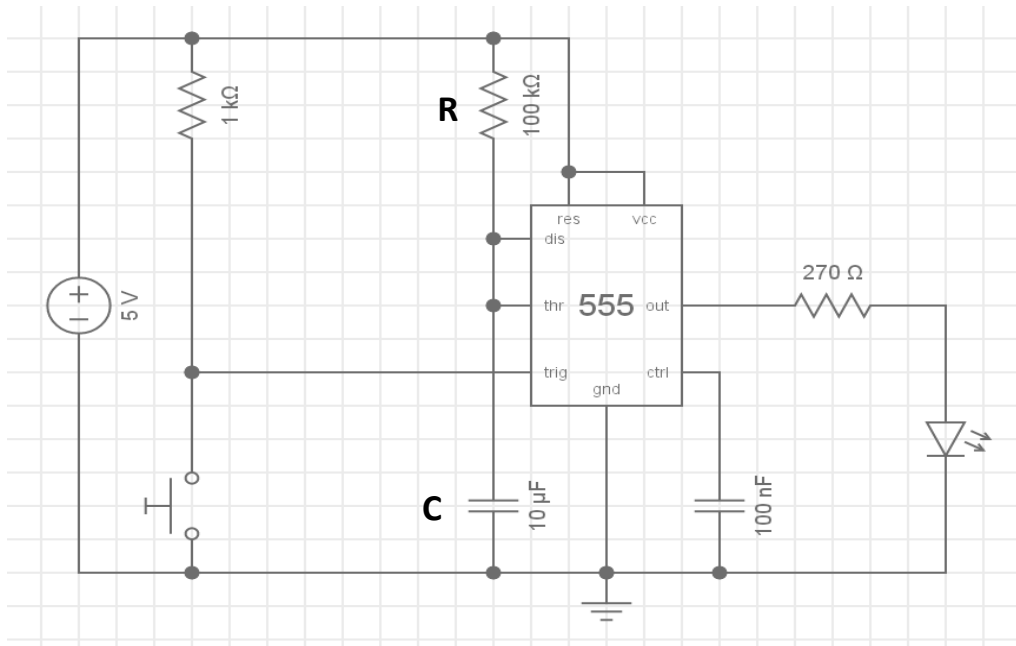


2. (5 points) Calculate  $T_{ON}$  for the circuit pictured above.
3. (5 points) Construct the above circuit and test it to be sure it functions as expected.  
Instructor sign-off \_\_\_\_\_
4. (2 points) Measure  $T_{ON}$  and record it below.
5. (5 points) Replace  $R$  with a  $1\text{ M}\Omega$  resistor. Calculate  $T_{ON}$ .
6. (2 points) Measure  $T_{ON}$  and record it below.
7. (2 points) Are the measured  $T_{ON}$  values as expected in steps 4 and 6? If they are significantly different, double check the wiring and component values.

### Section III: Astable

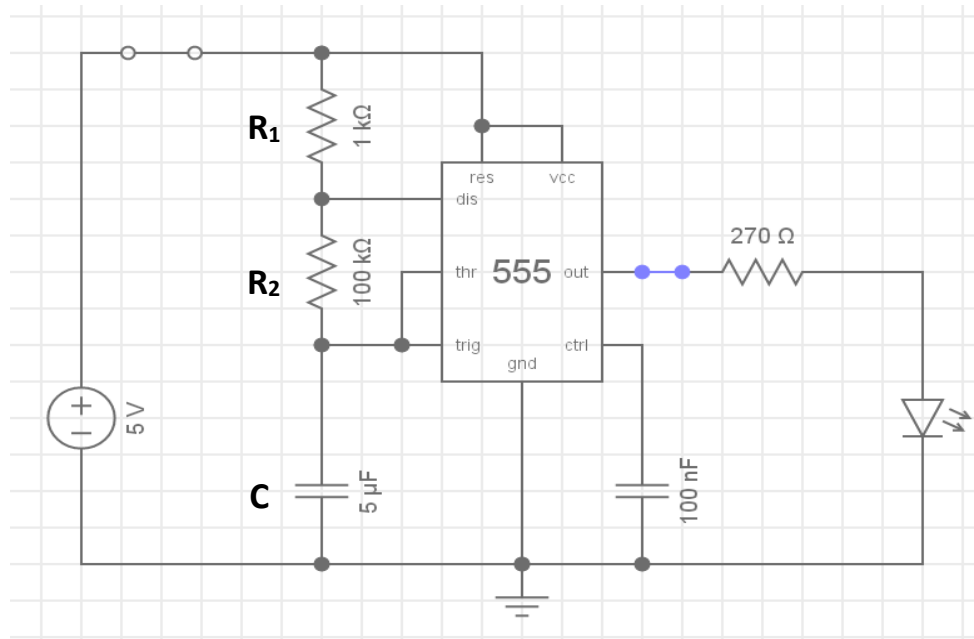1. The following 555 circuit is for an astable (no stable state) output. When powered, the operating frequency (in Hz) is calculated as follows:

$$F = \frac{1}{T_{ON} + T_{OFF}},$$

$$\text{where } T_{ON} = 0.693 * (R_1 + R_2)C \text{ and } T_{OFF} = 0.693 * R_2C$$



2. (5 points) Calculate the operating frequency for the circuit pictured above.
3. (5 points) Construct the circuit and test it to be sure it functions as expected.  
Instructor sign-off \_\_\_\_\_
4. (5 points) Connect the output to an oscilloscope and measure the frequency.
5. (5 points) Replace  $R_2$  with a 10 kΩ resistor. Calculate the new operating frequency.
6. (5 points) Measure the operating frequency and record it below.
7. (2 points) Are the measured frequencies as expected? If not, why?

#### Section IV: Postlab

1. (3 points) List three applications for a 555 timer.
2. (3 points) How are RC time constants used to control the frequency or  $T_{ON}$  of a 555 timer circuit?
3. (5 points) You have an application that requires an output pulse of 60 seconds. Using a  $1000\ \mu\text{F}$  capacitor, calculate a resistor value that will meet the circuit requirements.
4. (5 points) You have an application that requires an operating frequency of 60 Hz. Using  $R_1 = 1\text{k}\Omega$  and  $R_2 = 100\text{k}\Omega$ , calculate a capacitor value that will meet the circuit requirements.
5. (8 points) If  $R_1 = R_2 = 1\text{k}\Omega$ , and  $C = 5\ \mu\text{F}$ , calculate the following:

$T_{ON}$ :

$T_{OFF}$ :

Frequency:

Draw a picture of what the waveform would look like. Is time on equal to time off?

Total Score:          /90 points