

EET103 Formula Sheet

1. Ohm's Law

$$V = I \times R$$

Rearranged Forms:

$$I = V / R \quad R = V / I$$

2. Power Formulas

$$P = V \times I$$

Where:

- P = power (watts, W)

Algebraic Variations:

$$P = I^2 \times R \quad P = V^2 / R$$

Rearranged Forms:

$$I = P / V \quad V = P / I \quad R = V^2 / P$$

3. Kirchhoff's Voltage Law (KVL)

The sum of voltages around any closed loop equals zero.

$$\Sigma V = 0$$

Example:

$$V_s - V_1 - V_2 - V_3 = 0$$

$$\text{Or equivalently: } V_s = V_1 + V_2 + V_3$$

4. Kirchhoff's Current Law (KCL)

The sum of currents entering a node equals the sum of currents leaving the node.

$$\Sigma I_{\text{in}} = \Sigma I_{\text{out}}$$

$$\text{Example: } I_T = I_1 + I_2 + I_3$$

5. Metric Prefixes and Conversions

Prefix	Symbol	Multiplier	Power of 10
Mega	M	1,000,000	10^6
Kilo	k	1,000	10^3
Base Unit	-	1	10^0
Milli	m	0.001	10^{-3}
Micro	μ	0.000001	10^{-6}

Conversions:

$$1 \text{ k}\Omega = 1,000 \Omega \quad 1 \text{ mA} = 0.001 \text{ A} \quad 1 \mu\text{A} = 0.000001 \text{ A}$$

Where:

- V = voltage (volts, V)
- I = current (amperes, A)
- R = resistance (ohms, Ω)